

Tutorial-6 SolutionAns. $Z_0 = 0.32 \Omega$

(a) Reflection coefficient at the load

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{30 - 20j - 50}{30 - 20j + 50} = 0.343 \angle -$$

$$(b) SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.343}{1 - 0.343} = 2.044$$

$$(c) Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \phi}{Z_0 + jZ_L \tan \phi}$$

$$= 50 \frac{30 - 20j + j50(-3.07)}{50 + j(30 - 20j)(-3.07)}$$

$$= 50 \frac{30 - 20j - 153.5j}{50 - 61.4 - 92.1j} = 90$$

$$(d) \quad \Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{90.78 + 27.52j}{90.78 + 27.52j}$$

$\Gamma_{in} = 0.343 \angle 22.92^\circ$

Aus 2

$$Z_{SC} = Z_{in} \mid = jZ_0 \tan \beta \quad - \textcircled{1}$$

$Z_L = 0$


$$Z_{OC} = Z_{in} \mid = -jZ_0 \cot \beta \quad - \textcircled{2}$$

$Z_L = \infty$

Multiply $\textcircled{1}$ and $\textcircled{2}$

$$Z_{SC} \cdot Z_{OC} = Z_0^2$$

Aus 3

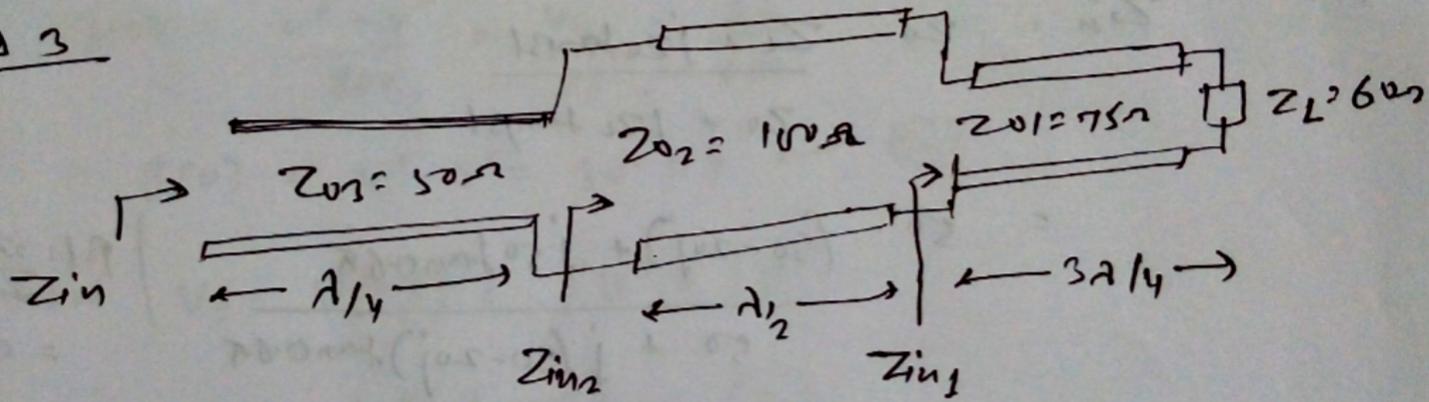


$$Z_{in1} : \frac{Z_{in1}^2}{Z_L} = \frac{75 \times 75}{60} = 93.75 \Omega$$

$$Z_{in2} = Z_{in1} = 93.75 \Omega$$

$$Z_{in} = \frac{Z_{in2}^2}{Z_{in2}} = \frac{Z_{in2}^2}{Z_{in2}} = \frac{50 \times 50}{93.75} =$$

$$Z_{in} = 26.67 \Omega$$

Aus 4

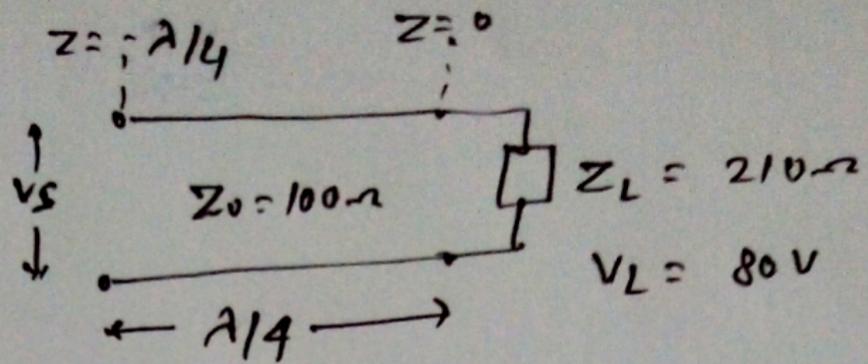

$$V_S = ?$$

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

$$I(z) = \frac{V^+ e^{-j\beta z} - V^- e^{j\beta z}}{Z_0}$$

$$V(0) = V_L = V^+ + V^- = 80 \quad \rightarrow \quad ①$$

$$I(0) = \frac{V^+ - V^-}{Z_0} = \frac{V_L}{Z_L} = \frac{80}{210}$$

$$\therefore I(0) = V^+ - V^- = 38.09 \quad \rightarrow \quad ②$$

Now $V_S = V\left(-\frac{\lambda}{4}\right) = jV^+ - jV^-$

$$V_S = j(V^+ - V^-) \quad \rightarrow \quad ③$$

from ② and ③

$$V_S = 38.09j = 38.09 \angle 90^\circ V$$