

# EE301: Electromagnetic Waves

## Tutorial 6 - Part B

October 11, 2018

## Problem 1: Smith chart

*A lossless line having an air dielectric has a characteristic impedance,  $Z_0$  of  $400\Omega$ . The line is operating at  $200\text{MHz}$  and input impedance,  $Z_{in} = (200 - j200)\Omega$ . Use analytic methods and the Smith chart to find:*

- (a) Input admittance*
- (b) Input VSWR*
- (c) Load impedance if the line is  $1\text{m}$  long*
- (d) VSWR at the load*
- (e) The distance from the load to nearest voltage maximum*

## Problem 1a: Analytical solution

(a) Input admittance

$$Y_{in} = \frac{1}{Z_{in}}$$

$$\Rightarrow Y_{in} = \frac{1}{200 - j200} = (2.5 \times 10^{-3} + j2.5 \times 10^{-3}) \text{ S}$$

# Problem 1a: Solution

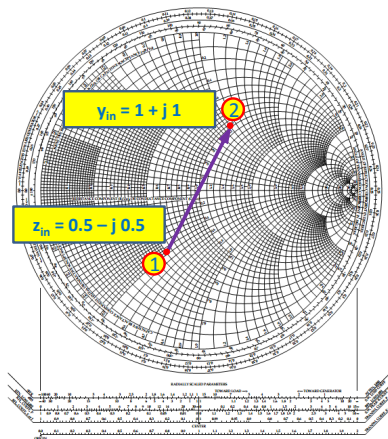


Figure: Input admittance calculation using Smith chart

## Problem 1b: Analytical solution

(b) Input *VSWR*

Input reflection coefficient,  $\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$

$$\Rightarrow \Gamma_{in} = -0.2 + j0.4 = 0.447 \angle 116.56^\circ$$

Input *VSWR*,  $VSWR_{in} = \frac{1 + |\Gamma_{in}|}{1 - |\Gamma_{in}|}$

$$\Rightarrow VSWR_{in} = 2.617$$

# Problem 1b: Solution

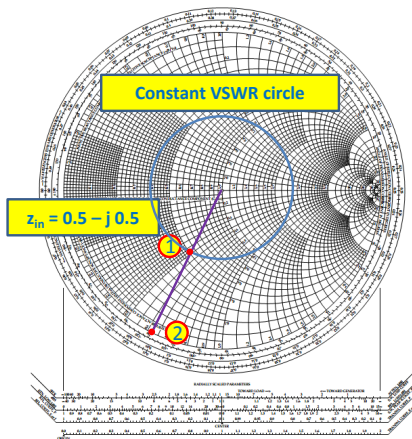


Figure: Input VSWR calculation using Smith chart

## Problem 1c: Analytical solution

(c) Load impedance

$$\text{Input impedance, } Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)}$$

$$\implies \text{Load impedance, } Z_L = Z_0 \frac{Z_{in} - jZ_0 \tan(\beta l)}{Z_0 - jZ_{in} \tan(\beta l)}$$

$$Z_L = (1040 + j69.8)\Omega$$

## Problem 1c: Solution

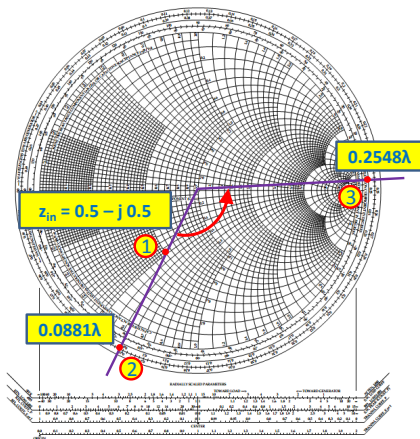


Figure: Load impedance calculation using Smith chart



# Problem 1c: Solution

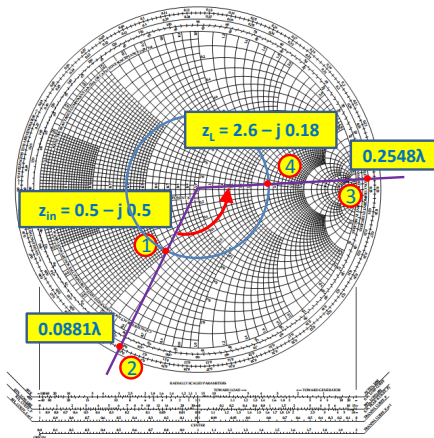


Figure: Load impedance calculation using Smith chart

## Problem 1d: Analytical solution

(d)  $VSWR$  at the load

Load reflection coefficient,  $\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$

$$\Rightarrow \Gamma_L = 0.446 - j0.268 = 0.447 \angle 3.45^\circ$$

Load  $VSWR$ ,  $VSWR_L = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$

$$\Rightarrow VSWR_L = 2.617$$

## Problem 1e: Analytical solution

(e) Nearest voltage maximum

$$I_{max} = -\frac{\phi}{2\beta} = -\frac{\lambda\phi}{4\pi} = -7.2mm$$

Note:  $\phi$  should be in radian

# Problem 1e: Solution

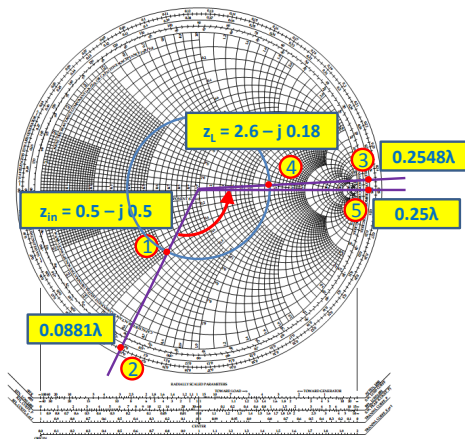


Figure: Distance to the nearest voltage maximum

THANK YOU